

Index

No.	Name of Experiment	Page
01	Study of different equipments in circuit lab.	
02	Verification of Ohm's law.	
03	Verification of Kirchhoff's law.	
04	Verification of superposition theorem.	
05	Verification of Thevenin's theorem.	